



Rewarding Learning

General Certificate of Secondary Education
2023

Centre Number

--	--	--	--	--

Candidate Number

--	--	--	--	--

Double Award Science: Physics

Unit 7: Practical Skills

Booklet A
Foundation Tier

[GDW71]



GDW71

TIME

1 hour.

INSTRUCTIONS TO CANDIDATES

Write your Centre Number and Candidate Number in the spaces provided at the top of this page.

Write your answers in the spaces provided in this question paper.

Answer **all** parts of Question 1.

INFORMATION FOR CANDIDATES

The total mark for this paper is **15**.

Figures in brackets printed down the right-hand side of pages indicate the marks awarded to each question or part of the question.

Follow all health and safety instructions.

You may use a ruler and a calculator if required.

The apparatus and materials required to complete the task(s) are provided.

For Examiner's
use only

Question Number	Marks
1	

Total Marks	
----------------	--

Examiner Only	
Marks	Remark

-
- The diagram shows a series circuit for measuring the resistance of a wire. The components are connected as follows:
- Power supply:** A rectangular box at the top right, labeled "Power supply".
 - Ammeter (A):** A circle with the letter "A" inside, connected in series with the power supply.
 - Variable resistor:** A rectangle with a diagonal arrow pointing through it, connected in series with the ammeter.
 - Wire:** A long horizontal rectangle at the bottom, labeled "Wire".
 - Voltmeter (V):** A circle with the letter "V" inside, connected in parallel across the wire.
- The circuit is completed by connecting the other terminal of the variable resistor to one end of the wire, and the other end of the wire back to the power supply.

(a) Turn on the power supply and adjust the variable resistor until the ammeter reads approximately 0.20A.

The current should be recorded to 2 decimal places and the voltage to 1 decimal place.

Obtain a range of currents and corresponding voltages and record these in the table.

Current / A	Voltage / V	Voltage / Current

You must complete the remainder of the paper on your own.

(e) What relationship between voltage and current does your graph indicate?

Circle your choice below.

direct proportion

**inverse (indirect)
proportion**

Give two reasons for your choice.

1. _____

2. _____ [2]

THIS IS THE END OF THE QUESTION PAPER

Examiner Only	
Marks	Remark

Permission to reproduce all copyright material has been applied for.
In some cases, efforts to contact copyright holders may have been unsuccessful and CCEA
will be happy to rectify any omissions of acknowledgement in future if notified.



General Certificate of Secondary Education
2023

Double Award Science Physics

Unit 7: Practical Skills

Booklet A

Foundation Tier

[GDW71]

APPARATUS AND MATERIALS LIST AND CONFIDENTIAL INSTRUCTIONS

To be accessed by Head of Department only

It is the responsibility of the centre to ensure that appropriate risk assessments are carried out for all practical skills assessments.

Apparatus and Materials list for P7A F and P7A H – Summer 2023


The experiment requires

- Power supply unit (PSU) capable of producing 6V.
- Variable resistor (rheostat) * – see note below.
- Analogue ammeter capable of reading up to $0.50\text{A} \pm 0.01\text{A}$ or digital ammeter reading to 2 decimal places.
- Analogue voltmeter capable of reading $0 - 5.0\text{V} \pm 0.1\text{V}$ or digital voltmeter reading to 1 decimal place.
- 28 SWG nichrome wire.
- Two crocodile clips.
- Metre rule.
- A minimum of 6 connecting wires.

Cut a length of nichrome wire and attach one crocodile clip at each end so that there is a length of **100 cm between the clips**. The wire should be taped to the metre rule.

*The Examining Team does not wish to put schools to the expense of ordering specific variable resistors. For your information, the Team used a 20Ω variable resistor.

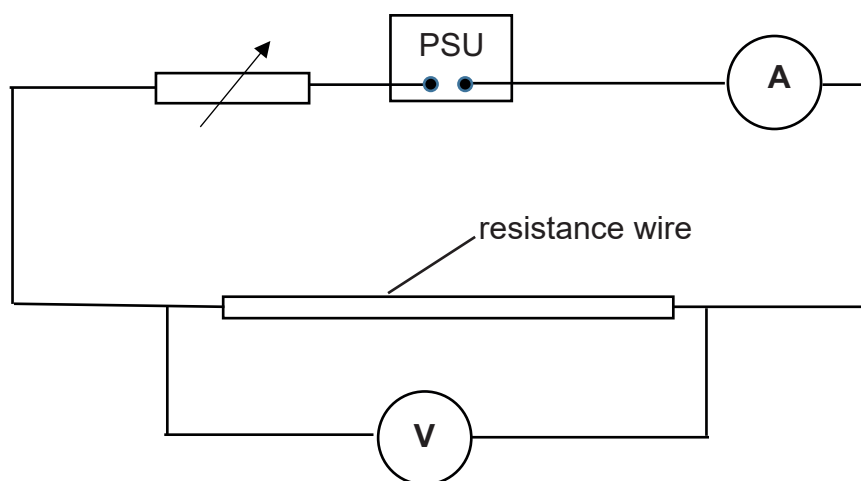In setting up the circuit below, therefore, the supervisor should ensure that the output voltage and variable resistor settings are such that a range of five current readings up to a maximum of 0.50A can be obtained.



The PSU should now be taped over so that the candidate cannot change the setting.

Health and safety

The power supply should be switched off before the candidate starts the experiment.